





Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Understanding Closed Circuit

(I). Record different types of closed circuits according to experiments and activities in class.

1. This is a \_\_\_\_\_ circuit.

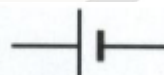Physical Representation

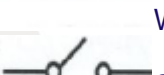
Circuit Diagram	
	<p><u>Legend</u></p> <p> Battery</p> <p> Bulb</p> <p> Wire</p> <p> Switch</p>

Here are defects of such closed circuit: \_\_\_\_\_

\_\_\_\_\_

2. This is a \_\_\_\_\_ circuit.

Physical Representation

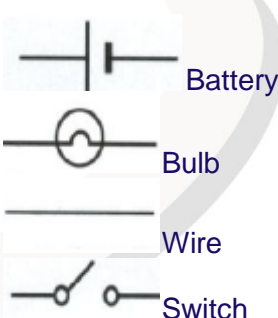Circuit Diagram	
	<p><u>Legend</u></p>  <p>Battery</p> <p>Bulb</p> <p>Wire</p> <p>Switch</p>

Here are the merits of such closed circuit: \_\_\_\_\_


\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

(II). Is series or parallel closed circuit used in the power supply system of a common household? Try to state your ideas in detail.

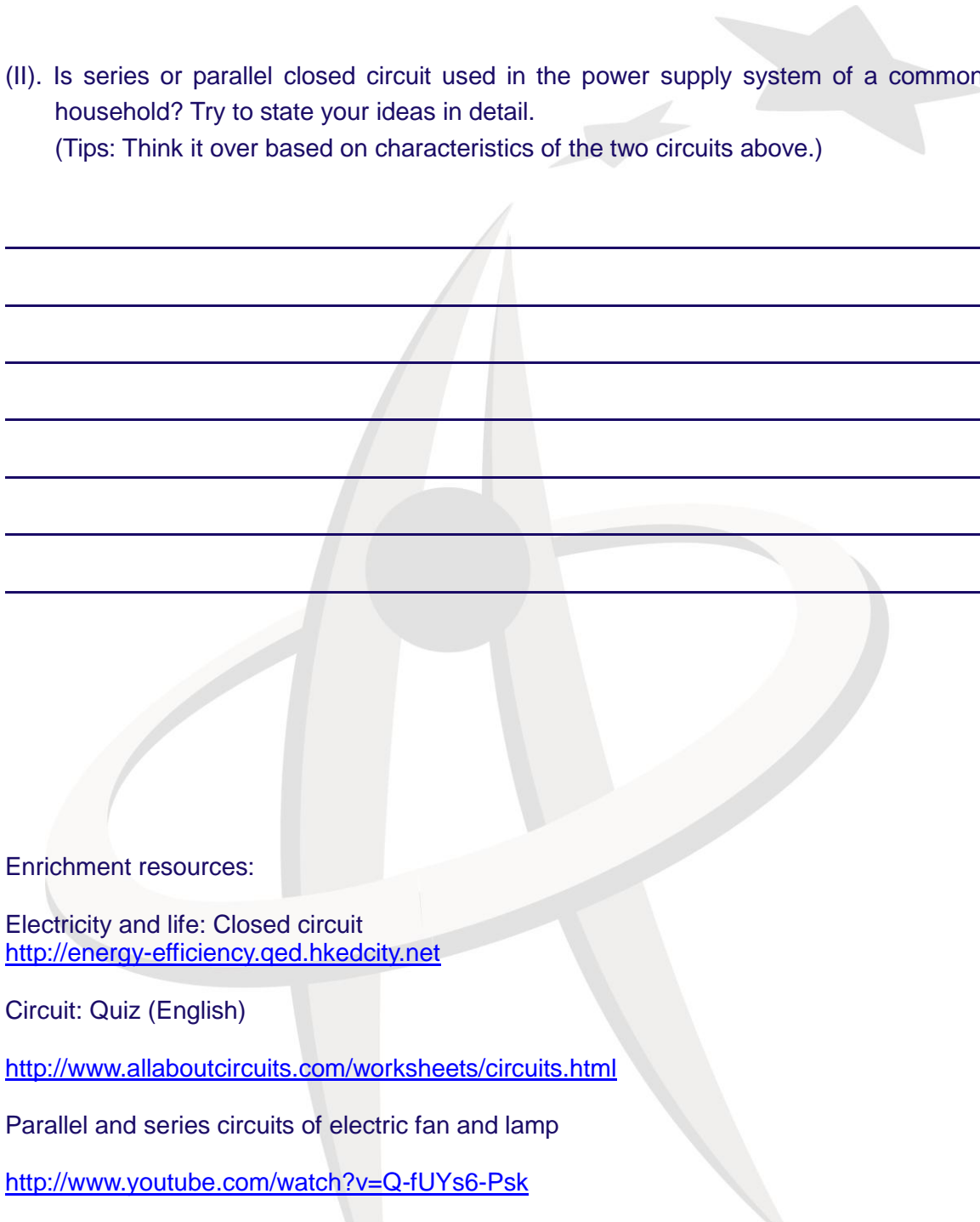(Tips: Think it over based on characteristics of the two circuits above.)



---

---

---

---

---

---

---

---

Enrichment resources:

Electricity and life: Closed circuit  
<http://energy-efficiency.qed.hkedcity.net>

Circuit: Quiz (English)

<http://www.allaboutcircuits.com/worksheets/circuits.html>

Parallel and series circuits of electric fan and lamp

<http://www.youtube.com/watch?v=Q-fUYs6-Psk>